


ECEN 714: Submission for LAB 1

Manav Gurumoorthy
830000011

Contents (Schematic, Testbench, Simulation results and Symbols)

1. Full adder
2. 4 bit adder
3. 4 bit register
4. 8 bit pipelined adder.

Full adder schematic:

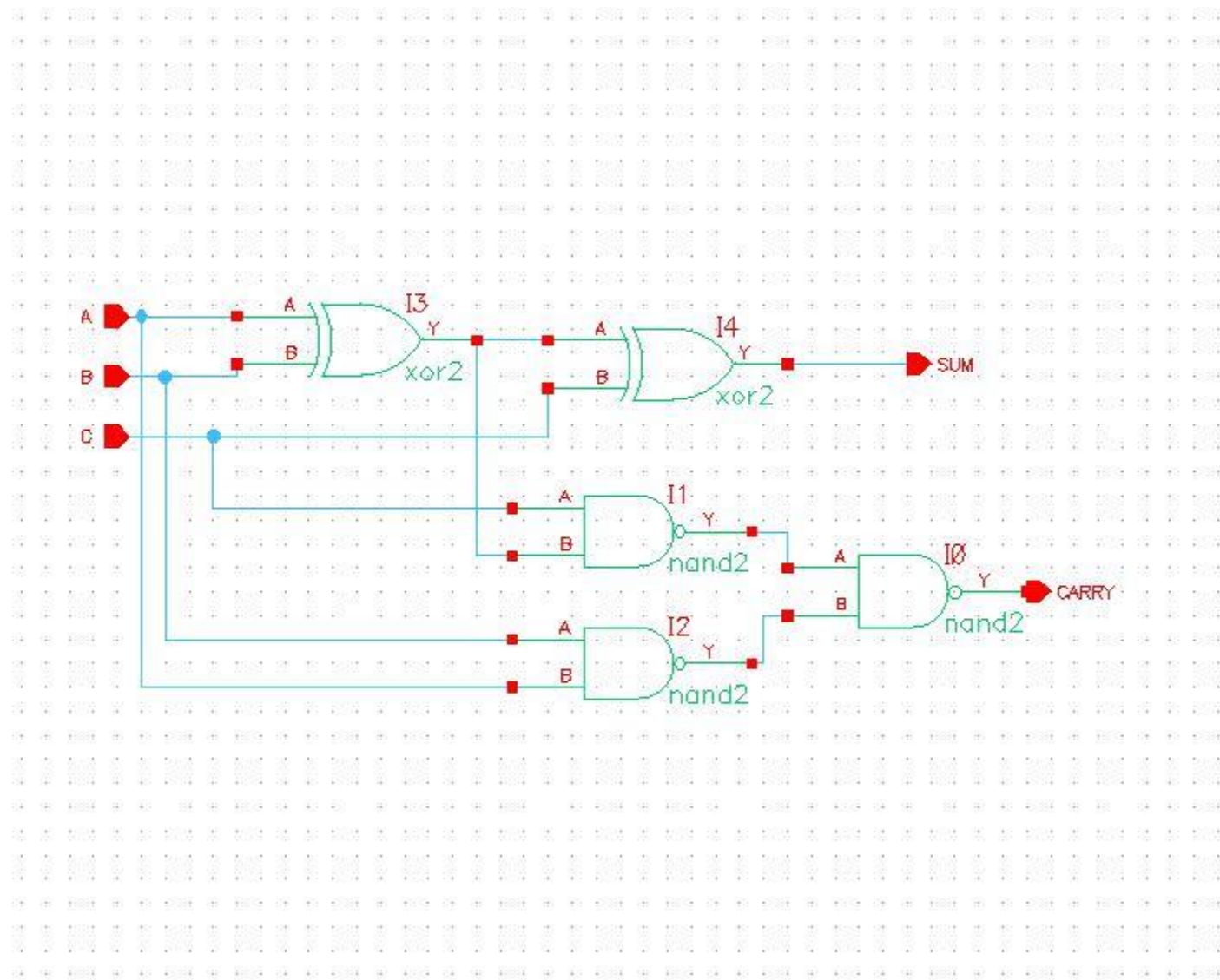

Testbench for full adder:

```
// Verilog stimulus file.
// Please do not create a module in this file.

// Default verilog stimulus.

initial
$monitor ($time," A=%b, B=%b, C=%b, SUM=%b, CARRY=%b", A, B, C, SUM, CARRY);

initial
begin

    A = 1'b0;
    B = 1'b0;
    C = 1'b0;

#50 A=1'b0; B=1'b0; C=1'b1;          //ABC=001
#50 A=1'b0; B=1'b1; C=1'b0;          //ABC=010
#50 A=1'b0; B=1'b1; C=1'b1;          //ABC=011
#50 A=1'b1; B=1'b0; C=1'b0;          //ABC=100
#50 A=1'b1; B=1'b0; C=1'b1;          //ABC=101
#50 A=1'b1; B=1'b1; C=1'b0;          //ABC=110
#50 A=1'b1; B=1'b1; C=1'b1;          //ABC=111
end
```

Simulation output for Full adder:

```
TOOL: ncxlmode    15.20-s077: Started on Sep 06, 2019 at 12:52:59 CDT
ncxlmode
+delay_mode_path
+typdelays
-l
simout.tmp
/home/grads/m/mana/ecen454/Lab1/fulladder_run1/testfixture.template
-f /home/grads/m/mana/ecen454/Lab1/fulladder_run1/verilog.inpfiles
```


```
    /opt/coe/ncsu/ncsu-cdk-1.6.0.beta/lib/NCSU_Digital_Parts/xor2/functional/verilog.v
    /opt/coe/ncsu/ncsu-cdk-1.6.0.beta/lib/NCSU_Digital_Parts/nand2/functional/verilog.v
    ihnl/cds0/netlist
+nostdout
+nocopyright
+ncvlogargs+" -neverwarn -nostdout -nocopyright "
+ncelabargs+" -neg_tchk -nonotifier -sdf_NOCheck_celltype -access +r -pulse_e 100 -pulse_r 100 -neverwarn -
timescale 1ns/1ns -nostdout -nocopyright"
+ncsimargs+" -neverwarn -nocopyright -gui -input /home/grads/m/mana/ecen454/Lab1/fulladder_run1/.simTmpNCCmd "
+mpssession+virtuosol87265
+mpshost+n01-zeus.olympus.ece.tamu.edu
```

```
-----
Relinquished control to SimVision...
ncsim>
ncsim> source /opt/coe/cadence/INCISIVE152/tools/inca/files/ncsimrc
ncsim> database -open shmWave -shm -default -into shm.db
Created default SHM database shmWave
ncsim> probe -create -shm test -all -depth 1
Created probe 1
ncsim> run
```


```
    0 A=0, B=0, C=0, SUM=0, CARRY=0
    50 A=0, B=0, C=1, SUM=1, CARRY=0
   100 A=0, B=1, C=0, SUM=1, CARRY=0
   150 A=0, B=1, C=1, SUM=0, CARRY=1
   200 A=1, B=0, C=0, SUM=1, CARRY=0
   250 A=1, B=0, C=1, SUM=0, CARRY=1
   300 A=1, B=1, C=0, SUM=0, CARRY=1
   350 A=1, B=1, C=1, SUM=1, CARRY=1
```

```
ncsim> ^C
ncsim> exit
TOOL: ncxlmode 15.20-s077: Exiting on Sep 06, 2019 at 12:57:12 CDT (total: 00:04:13)
```

Symbol for Full adder:

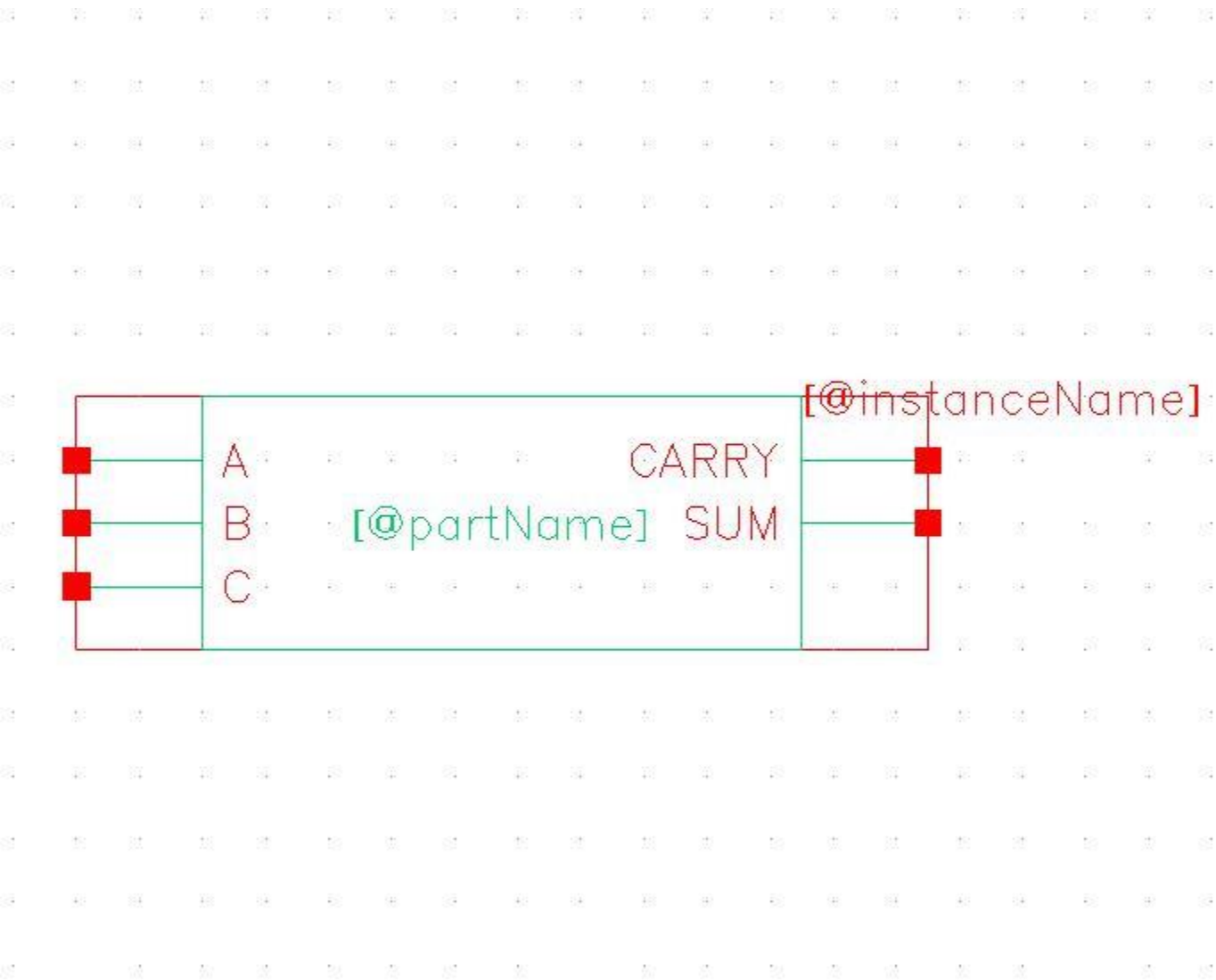

4 Bit adder schematic:

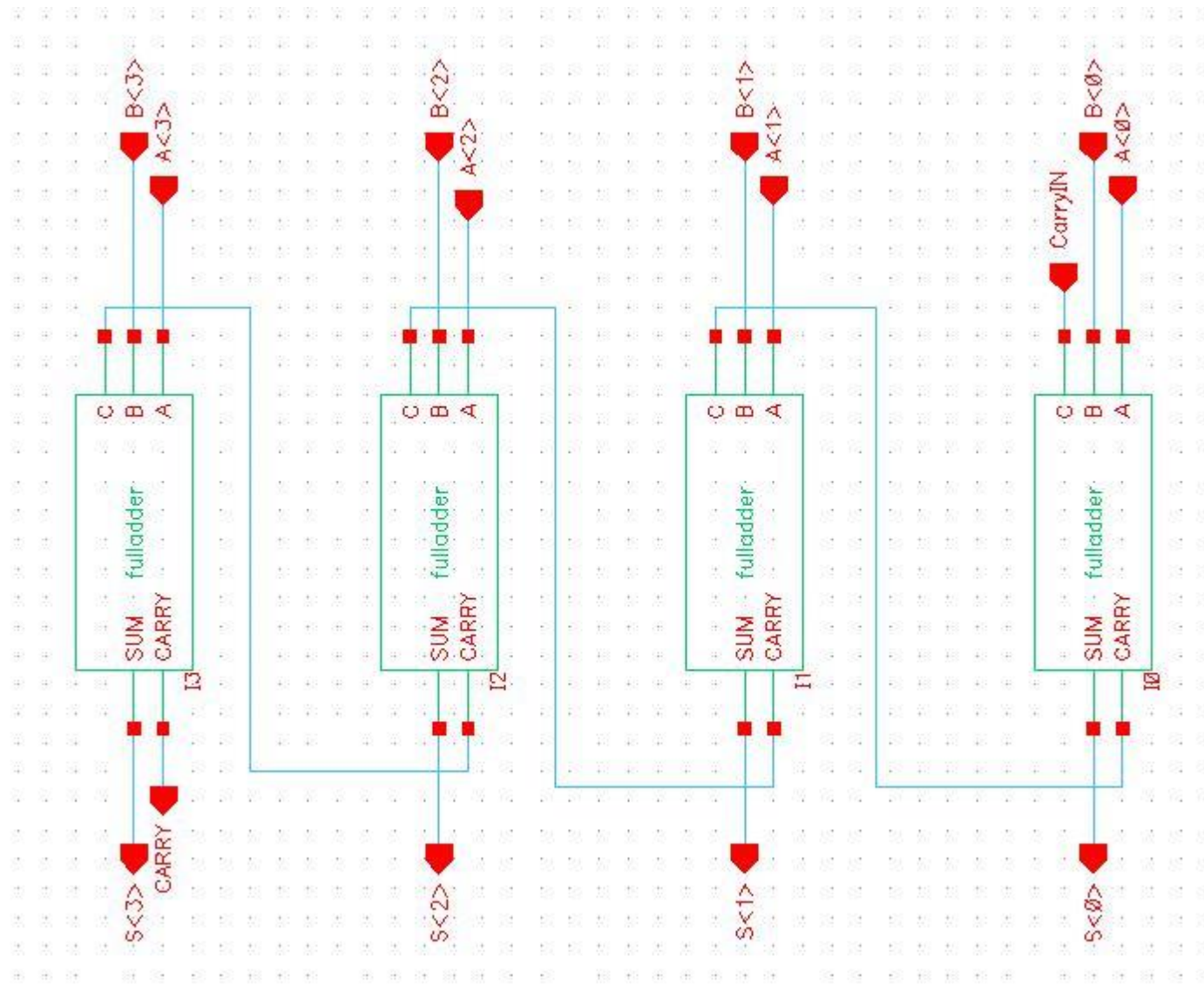

Test bench for the 4 bit adder:

```
// Verilog stimulus file.
// Please do not create a module in this file.

// Default verilog stimulus.

initial
$monitor ($time," A[0:3]=%b, B[0:3]=%b,CarryIN=%b, S[0:3]=%b, CARRY=%b", A[0:3], B[0:3], CarryIN, S[0:3], CARRY);

initial
begin

    A[0:3]=0;
    B[0:3]=0;

    CarryIN=1'b0;

#50 A[0:3]=3'b1111; B[0:3]=3'b1111; CarryIN=0;           //A = 1111 B = 1111 CarryIN=0
#50 A[0:3]=3'b1010; B[0:3]=3'b1010; CarryIN=1;          //A = 1010 B = 1010 CarryIN=1
#50 A[0:3]=3'b0101; B[0:3]=3'b0101; CarryIN=1;          //A = 0101 B = 0101 CarryIN=1
end
```

Simulation output for 4 bit adder:

```
TOOL: ncxlmode 15.20-s077: Started on Sep 09, 2019 at 12:51:58 CDT
ncxlmode
+delay_mode_path
+typdelays
-l
simout.tmp
/home/grads/m/mana/ecen454/Lab1/4BitAdder_run1/testfixture.template
-f /home/grads/m/mana/ecen454/Lab1/4BitAdder_run1/verilog.inpfiles
/opt/coe/ncsu/ncsu-cdk-1.6.0.beta/lib/NCSU_Digital_Parts/xor2/functional/verilog.v
/opt/coe/ncsu/ncsu-cdk-1.6.0.beta/lib/NCSU_Digital_Parts/nand2/functional/verilog.v
ihnl/cds0/netlist
ihnl/cds1/netlist
+nostdout
+nocopyright
```

```
+ncvlogargs+" -neverwarn -nostdout -nocopyright "  
+ncelabargs+" -neg_tchk -nonotifier -sdf_NOCheck_celltype -access +r -pulse_e 100 -pulse_r 100 -neverwarn -  
timescale 1ns/1ns -nostdout -nocopyright"  
+ncsimargs+" -neverwarn -nocopyright -gui -input /home/grads/m/mana/ecen454/Lab1/4BitAdder_run1/.simTmpNCCmd "  
+mpsession+virtuoso27094  
+mpshost+n01-zeus.olympus.ece.tamu.edu
```

```
-----  
Relinquished control to SimVision...
```


```
ncsim>  
ncsim> source /opt/coe/cadence/INCISIVE152/tools/inca/files/ncsimrc  
ncsim> database -open shmWave -shm -default -into shm.db  
Created default SHM database shmWave  
ncsim> probe -create -shm test -all -depth 1  
Created probe 1  
ncsim> run
```

```
0 A[0:3]=0000, B[0:3]=0000, CarryIN=0, S[0:3]=0000, CARRY=0  
50 A[0:3]=0111, B[0:3]=0111, CarryIN=0, S[0:3]=0011, CARRY=1  
100 A[0:3]=0010, B[0:3]=0010, CarryIN=1, S[0:3]=1001, CARRY=0  
150 A[0:3]=0101, B[0:3]=0101, CarryIN=1, S[0:3]=1010, CARRY=1
```


```
ncsim> ^C  
ncsim> exit
```

```
TOOL: ncxlmode 15.20-s077: Exiting on Sep 09, 2019 at 12:54:18 CDT (total: 00:02:20)
```


Symbol for 4 bit adder:

 

Schematic for 4 Bit Register:

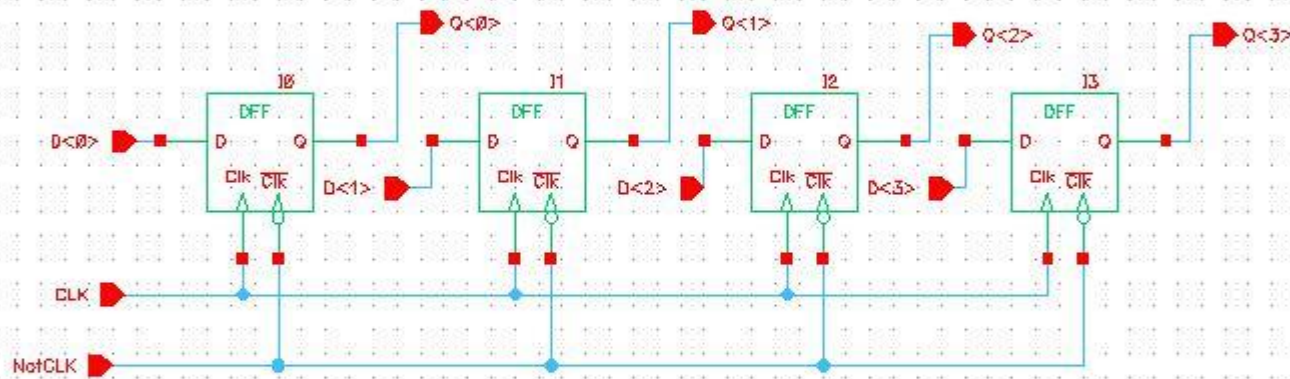

Test bench for the 4 bit register:

```
// Verilog stimulus file.
// Please do not create a module in this file.

// Default verilog stimulus.
initial begin
$monitor ($time," D[0:3]=%b, Q[0:3]=%b", D[0:3], Q[0:3]);
#500 $finish;
end

always begin
    CLK <= 1;
    NotCLK <= 0;
    #10
    CLK <= 0;
    NotCLK <= 1;
    #10;
end

initial begin
    //CLK = 1'b0;
    D[0] = 1'b0;
    D[1] = 1'b0;
    D[2] = 1'b0;
    D[3] = 1'b0;
    //NotCLK = 1'b0;
end

initial begin
    #40 @(posedge CLK) D[0:3]=4'b1111;
    #40 @(posedge CLK) D[0:3] = 4'b0101;
end
```

Simulation results for the 4 bit register:

TOOL: ncxlmode 15.20-s077: Started on Sep 09, 2019 at 17:28:05 CDT

ncxlmode

+delay_mode_path

+typdelays

-l

simout.tmp

/home/grads/m/mana/ecen454/Lab1/4BitRegister_run1/testfixture.template

-f /home/grads/m/mana/ecen454/Lab1/4BitRegister_run1/verilog.inpfiles

/opt/coe/ncsu/ncsu-cdk-1.6.0.beta/lib/NCSU_Digital_Parts/Dlatch/behavioral/verilog.v

ihnl/cds0/netlist

ihnl/cds1/netlist

+nostdout

+nocopyright

+ncvlogargs+" -neverwarn -nostdout -nocopyright "

+ncelabargs+" -neg_tchk -nonotifier -sdf_NOCheck_celltype -access +r -pulse_e 100 -pulse_r 100 -neverwarn -

timescale 1ns/1ns -nostdout -nocopyright"

+ncsimargs+" -neverwarn -nocopyright -gui -input /home/grads/m/mana/ecen454/Lab1/4BitRegister_run1/.simTmpNCCmd "

+mpssession+virtuosol33923

+mpshost+n01-zeus.olympus.ece.tamu.edu

Relinquished control to SimVision...

ncsim>

ncsim> source /opt/coe/cadence/INCISIVE152/tools/inca/files/ncsimrc

ncsim> database -open shmWave -shm -default -into shm.db

Created default SHM database shmWave

ncsim> probe -create -shm test -all -depth 1

Created probe 1

ncsim> run

0 D[0:3]=0000, Q[0:3]=xxxx

20 D[0:3]=0000, Q[0:3]=0000

40 D[0:3]=1111, Q[0:3]=1111

80 D[0:3]=0101, Q[0:3]=0101

Simulation complete via \$finish(1) at time 500 NS + 0


./testfixture.verilog:9 #500 \$finish;

ncsim> ^C

ncsim> exit

TOOL: ncxlmode 15.20-s077: Exiting on Sep 09, 2019 at 17:35:26 CDT (total: 00:07:21)

8 Bit adder schematic:

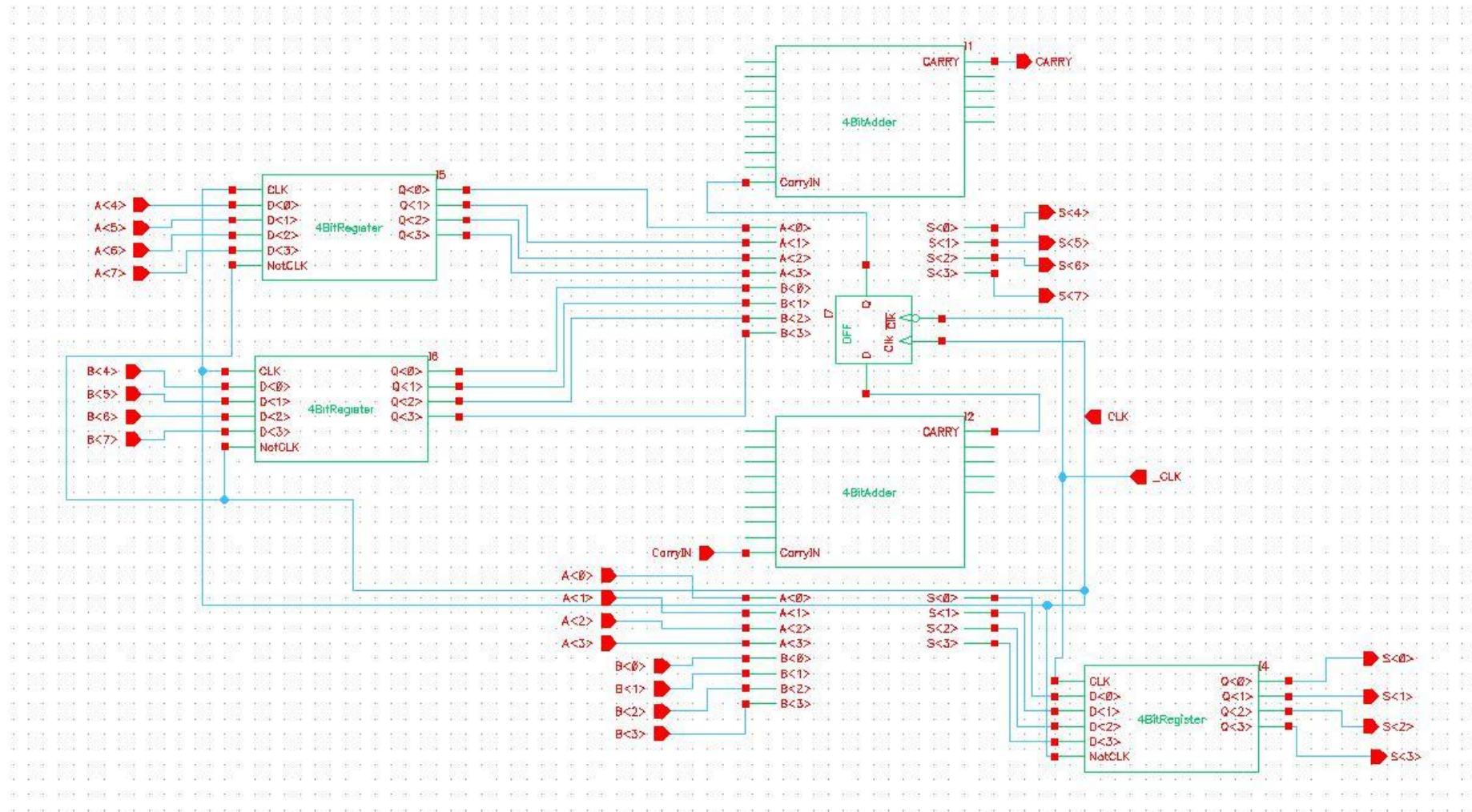

TEST BENCH FOR THE PIPELINED 8BIT ADDER:

```
// Verilog stimulus file.  
// Please do not create a module in this file.
```

```
// Default verilog stimulus.
```

```
initial begin
$monitor ($time," A[1:7]=%b, B[1:7]=%b, CarryIN=%b, S[1:7]=%b, CARRY=%b", A[0:7], B[0:7], CarryIN, S[0:7], CARRY);
```

```
end
```

```
initial
begin
    A[0] = 1'b0;
    A[1] = 1'b0;
    A[2] = 1'b0;
    A[3] = 1'b0;
    A[4] = 1'b0;
    A[5] = 1'b0;
    A[6] = 1'b0;
    A[7] = 1'b0;
    B[0] = 1'b0;
    B[1] = 1'b0;
    B[2] = 1'b0;
    B[3] = 1'b0;
    B[4] = 1'b0;
    B[5] = 1'b0;
    B[6] = 1'b0;
    B[7] = 1'b0;
    // CLK = 1'b0;
    CarryIN = 1'b0;
    //_CLK = 1'b0;
end
```

```
always begin
    CLK <= 1;
    _CLK <= 0;
    #10
    CLK <= 0;
    _CLK <= 1;
    #10;
end
```

```
initial begin
//i.> 01111110 +11100111 + 0 (Carry In)
```

```

@(posedge CLK)#20 A[0:3]=4'b0111; B[0:3]=4'b1110; CarryIN=0;
@(posedge CLK)#20 A[4:7]=4'b1110; B[4:7]=4'b0111;
#20;

//ii.> 11111111 + 00000000 + 1 (Carry In)
@(posedge CLK)#20 A[0:3]=4'b1111; B[0:3]=4'b0000; CarryIN=1;
@(posedge CLK)#20 A[4:7]=4'b1111; B[4:7]=4'b0000;
#20;

//iii.> 10101010 + 01010101 + 0 (Carry In)
@(posedge CLK)#20 A[0:3]=4'b0101; B[0:3]=4'b1010; CarryIN=0;
@(posedge CLK)#20 A[4:7]=4'b0101; B[4:7]=4'b1010;
#20;

//iv.> 10101010 + 01010101 + 1 (Carry In)
@(posedge CLK)#20 A[0:3]=4'b0101; B[0:3]=4'b1010; CarryIN=1;
@(posedge CLK)#20 A[4:7]=4'b0101; B[4:7]=4'b1010;
#20;

//v.> 11001100 + 00110011 + 0 (Carry In)
@(posedge CLK)#20 A[0:3]=4'b0011; B[0:3]=4'b1100; CarryIN=0;
@(posedge CLK)#20 A[4:7]=4'b0011; B[4:7]=4'b1100;
#20;

//vi.> 11001100 + 00110011 + 1 (Carry In)
@(posedge CLK)#20 A[0:3]=4'b0011; B[0:3]=4'b1100; CarryIN=1;
@(posedge CLK)#20 A[4:7]=4'b0011; B[4:7]=4'b1100;
#20;

end

```

OUTPUT OF SIMULATIONS FOR THE PIPELINED 8BIT ADDER:

TOOL: ncxlmode 15.20-s077: Started on Sep 09, 2019 at 19:48:45 CDT

```

ncxlmode
+delay_mode_path
+typdelays
-l
simout.tmp
/home/grads/m/mana/ecen454/Lab1/8BitPipeAdder_run1/testfixture.template
-f /home/grads/m/mana/ecen454/Lab1/8BitPipeAdder_run1/verilog.inpfiles
/opt/coe/ncsu/ncsu-cdk-1.6.0.beta/lib/NCSU_Digital_Parts/xor2/functional/verilog.v
/opt/coe/ncsu/ncsu-cdk-1.6.0.beta/lib/NCSU_Digital_Parts/nand2/functional/verilog.v

```

```

/opt/coe/ncsu/ncsu-cdk-1.6.0.beta/lib/NCSU_Digital_Parts/Dlatch/behavioral/verilog.v
ihnl/cds0/netlist
ihnl/cds1/netlist
ihnl/cds2/netlist
ihnl/cds3/netlist
ihnl/cds4/netlist
+nostdout
+nocopyright
+ncvlogargs+" -neverwarn -nostdout -nocopyright "
+ncelabargs+" -neg_tchk -nonotifier -sdf_NOCheck_celltype -access +r -pulse_e 100 -pulse_r 100 -neverwarn -
timescale 1ns/1ns -nostdout -nocopyright"
+ncsimargs+" -neverwarn -nocopyright -gui -input /home/grads/m/mana/ecen454/Lab1/8BitPipeAdder_run1/.simTmpNCCmd "
+mpsession+virtuosol91263
+mpshost+n01-zeus.olympus.ece.tamu.edu

```

```

-----
Relinquished control to SimVision...

```

```

ncsim>
ncsim> source /opt/coe/cadence/INCISIVE152/tools/inca/files/ncsimrc
ncsim> database -open shmWave -shm -default -into shm.db
Created default SHM database shmWave
ncsim> probe -create -shm test -all -depth 1
Created probe 1
ncsim> run

```

```

    0 A[1:7]=00000000, B[1:7]=00000000, CarryIN=0, S[1:7]=xxxxxxx, CARRY=x
   10 A[1:7]=00000000, B[1:7]=00000000, CarryIN=0, S[1:7]=0000xxxx, CARRY=x
   20 A[1:7]=01110000, B[1:7]=11110000, CarryIN=0, S[1:7]=0000xxxx, CARRY=x
   30 A[1:7]=01110000, B[1:7]=11110000, CarryIN=0, S[1:7]=10101000, CARRY=0
   40 A[1:7]=01111110, B[1:7]=11100111, CarryIN=0, S[1:7]=10101000, CARRY=0
   70 A[1:7]=01111110, B[1:7]=11100111, CarryIN=0, S[1:7]=10100110, CARRY=1
   80 A[1:7]=11111110, B[1:7]=00000111, CarryIN=1, S[1:7]=10100110, CARRY=1
   90 A[1:7]=11111110, B[1:7]=00000111, CarryIN=1, S[1:7]=00000110, CARRY=1
  100 A[1:7]=11111111, B[1:7]=00000000, CarryIN=1, S[1:7]=00000110, CARRY=1
  130 A[1:7]=11111111, B[1:7]=00000000, CarryIN=1, S[1:7]=00000000, CARRY=1
  140 A[1:7]=01011111, B[1:7]=10100000, CarryIN=0, S[1:7]=00001111, CARRY=0
  150 A[1:7]=01011111, B[1:7]=10100000, CarryIN=0, S[1:7]=11111111, CARRY=0
  160 A[1:7]=01010101, B[1:7]=10101010, CarryIN=0, S[1:7]=11111111, CARRY=0
  200 A[1:7]=01010101, B[1:7]=10101010, CarryIN=1, S[1:7]=11110000, CARRY=1
  210 A[1:7]=01010101, B[1:7]=10101010, CarryIN=1, S[1:7]=00000000, CARRY=1
  260 A[1:7]=00110101, B[1:7]=11001010, CarryIN=0, S[1:7]=00001111, CARRY=0
  270 A[1:7]=00110101, B[1:7]=11001010, CarryIN=0, S[1:7]=11111111, CARRY=0
  280 A[1:7]=00110011, B[1:7]=11001100, CarryIN=0, S[1:7]=11111111, CARRY=0
  320 A[1:7]=00110011, B[1:7]=11001100, CarryIN=1, S[1:7]=11110000, CARRY=1

```



```

330 A[1:7]=00110011, B[1:7]=11001100, CarryIN=1, S[1:7]=00000000, CARRY=1
Simulation interrupted at 88334850 NS + 0
ncsim> ^C
ncsim> exit
TOOL: ncxlmode 15.20-s077: Exiting on Sep 09, 2019 at 19:50:19 CDT (total: 00:01:34)

```

8 Bit adder symbol:

