

ECEN 714: Submission for LAB 7b

Manav Gurumoorthy
830000011

Contents (Schematic, Layout, DRC and LVS for the 6-bit Pipelined Adder and H-clock tree and Post Layout Simulation)

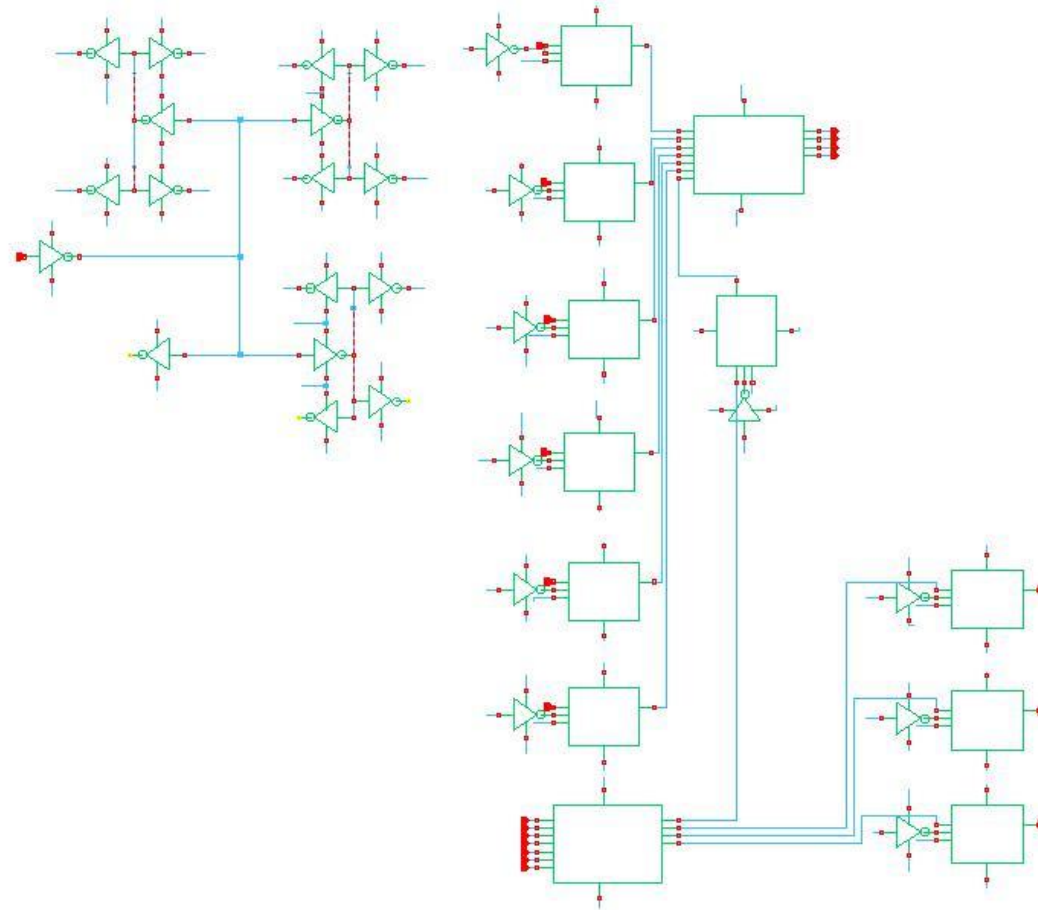


Figure 2: Schematic of the 6-bit Pipelined adder

Layout

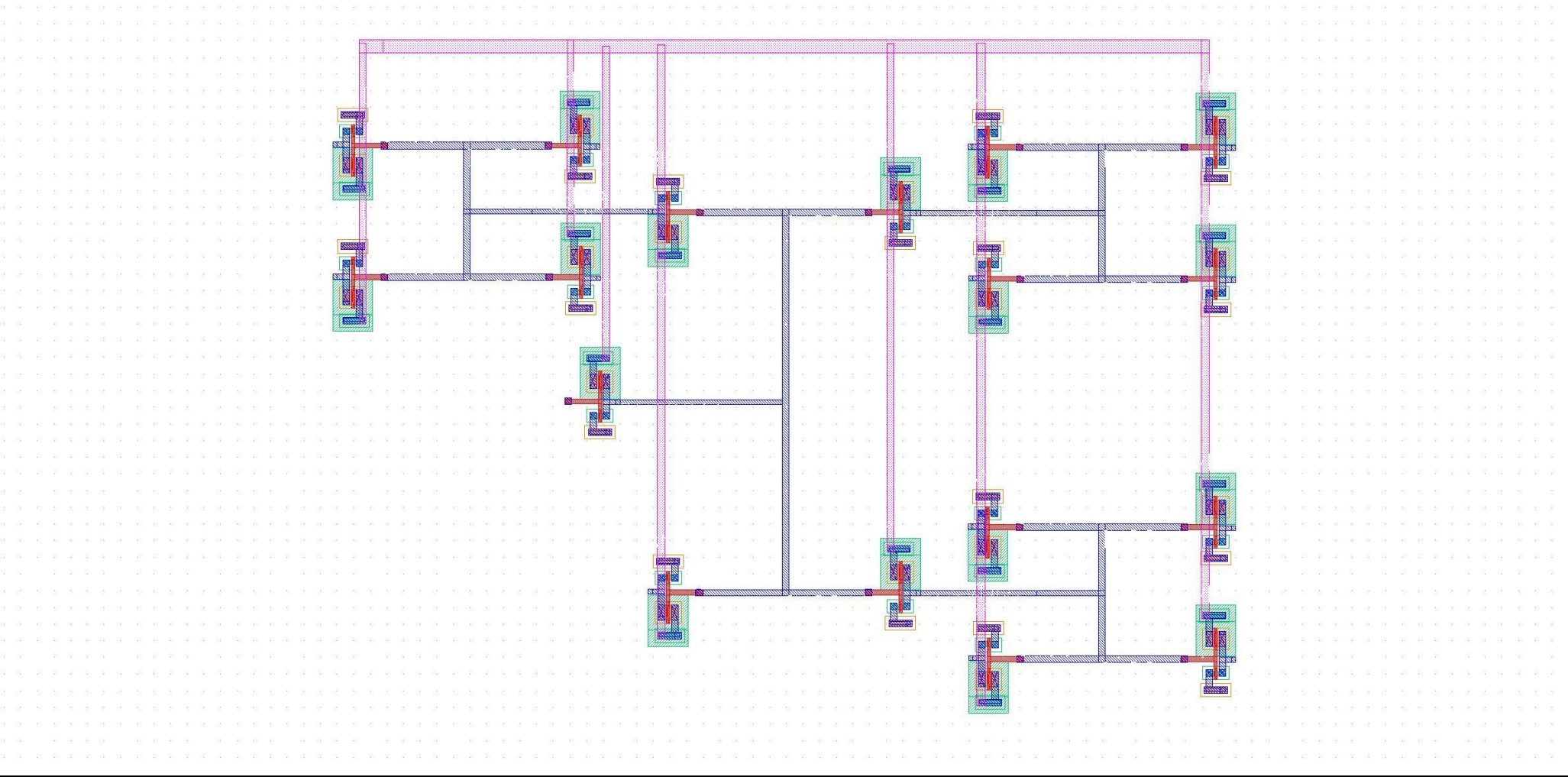


Figure 3: Layout for the H-tree clock distribution network

 


Figure 4: Layout for the 6-bit Pipelined Adder

 


Figure 5. Same layout (To show UIN)

Total Area of the Layout

Length	245
Breadth	233.65
Total Area	57244.25

DRC:

 


Figure 6. DRC results

LVS report:

@(#) \$CDS: LVS version 6.1.8-64b 10/01/2018 19:50 (ip-172-18-22-57) \$

Command line: /opt/coe/cadence/IC618/tools.lnx86/dfII/bin/64bit/LVS -dir /home/grads/m/mana/ecen454/Lab1/LVS -l -s -t /home/grads/m/mana/ecen454/Lab1/LVS/layout /home/grads/m/mana/ecen454/Lab1/LVS/schematic

Like matching is enabled.

Net swapping is enabled.

Using terminal names as correspondence points.

Compiling Diva LVS rules...

Net-list summary for /home/grads/m/mana/ecen454/Lab1/LVS/layout/netlist

count

243	nets
23	terminals
235	pmos
235	nmos

Net-list summary for /home/grads/m/mana/ecen454/Lab1/LVS/schematic/netlist

count

243	nets
23	terminals
235	pmos
235	nmos

Terminal correspondence points

N231	N58	Cout_out
N225	N42	GND
N236	N53	S0_out
N242	N50	S1_out
N223	N52	S2_out
N229	N0	S3_out
N235	N46	S4_out
N241	N56	S5_out
N240	N31	VDD
N233	N55	a0_in
N224	N45	a1_in
N237	N13	a2_in
N226	N60	a3_in
N238	N39	a4_in
N227	N47	a5_in
N239	N57	b0_in

N228	N48	b1_in
N220	N54	b2_in
N232	N41	b3_in
N222	N51	b4_in
N234	N43	b5_in
N221	N7	cin_in
N230	N26	clk

Devices in the netlist but not in the rules:

pcapacitor

Devices in the rules but not in the netlist:

cap nfet pfet nmos4 pmos4

The net-lists match.

	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	470	470
total	470	470
	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	243	243
total	243	243
	terminals	
un-matched	0	0
matched but		
different type	0	0
total	23	23

Probe files from /home/grads/m/mana/ecen454/Lab1/LVS/schematic

devbad.out:

netbad.out:

mergenet.out:

termbad.out:

prunenet.out:

prunedev.out:

audit.out:

Probe files from /home/grads/m/mana/ecen454/Lab1/LVS/layout

devbad.out:

netbad.out:

mergenet.out:


termbad.out:

prunenet.out:


prunedev.out:

audit.out:


6-bit Adder Layout:

 


Post Layout Simulation:

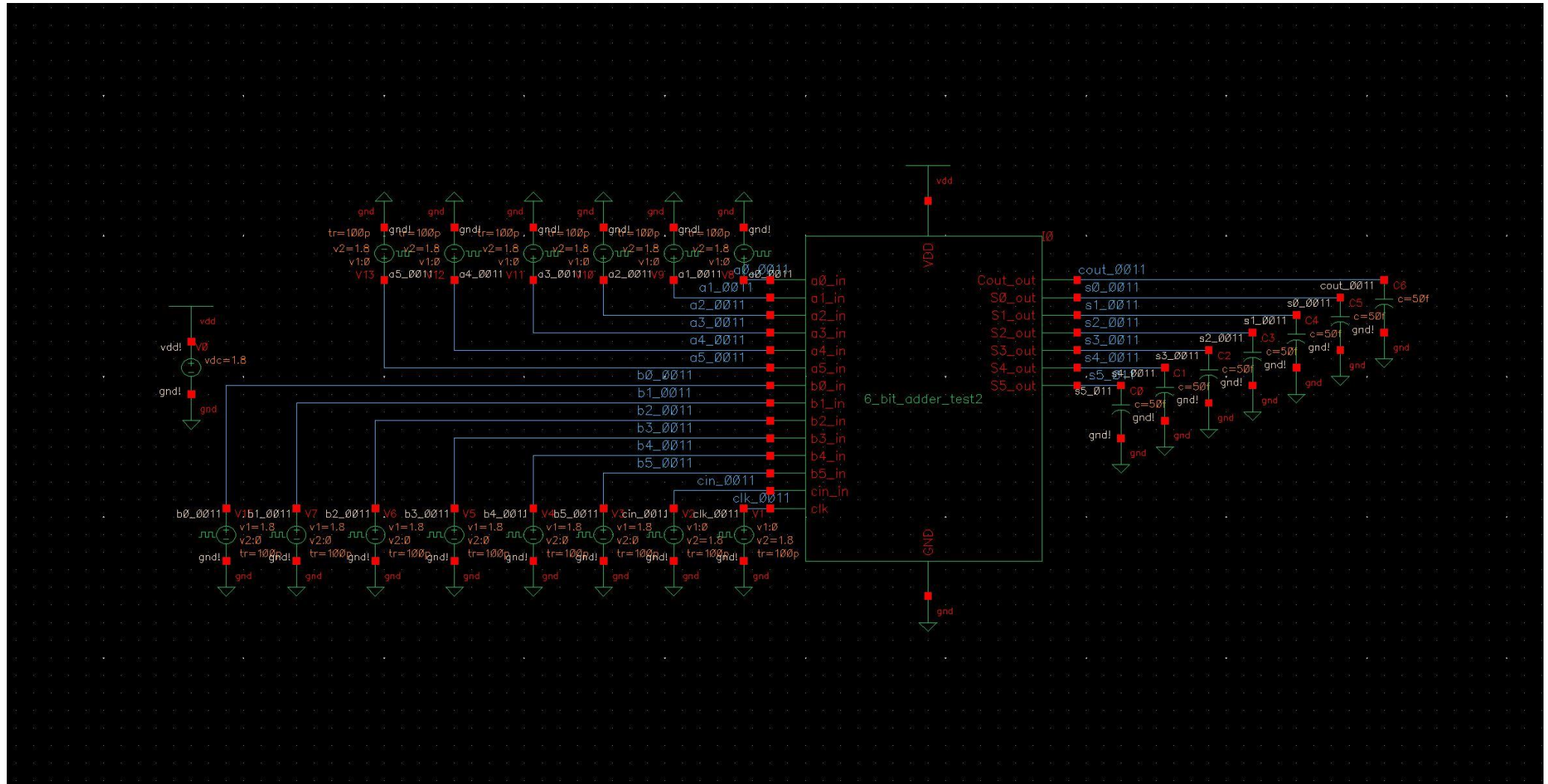

Input Vector 1: (30ns clock period)

 

Input Vector 2: (30ns clock period)

 


Input Vector 1: (Highest Performance)

Transient Response

Mon Nov 4 13:11:04
2019

1

 


Input Vector 2: (Highest Performance)

Transient Response

Mon Nov 4 13:29:27
2019

1

 

Calculations:

Input Vector 1	011110+ 111111+ 0
Max Period	1.9ns
Delay	5ns
Current	-1.38E-03
Voltage	1.8
Power	-0.0024858

Input Vector 2	0000000+111111+1
Max Period	1.9ns
Delay	5ns
Current	-1.41E-03
Voltage	1.8
Power	-0.0025452